

## Lab 7 Report

Berke Diler

2401503


## Introduction:

The goal of this project is to design a Fibonacci sequence calculator. Which will take a predefined value 'count' and then calculate the Fibonacci sequence until the sequence comes to the number of count. To give an example, if we define count=7. Then we will have the 7<sup>th</sup> value in the sequence which is the number 13.


The Fibonacci sequence: 1,1,2,3,5,8,13,21,34,55,89,144,233,377,610...

Sub-components of the project are a datapath and a finite state machine. The datapath is divided into sub-components aswell which are; a 2-to-4 line decoder, four 4-bit AND gates, five 4-bit 2-to-1 multiplexers, five 4-bit registers, two 4-bit 4-to-1 Multiplexers, and a 4-bit ALU. The FSM module is divided into two modules which are; the finite state machine itself, and a decoder for the finite state machine which decodes the signals from the finite state machine and directs the signals to the datapath with proper. The project and its sub-components are designed using the Verilog programming language.

The FSM State Diagram is as follows:

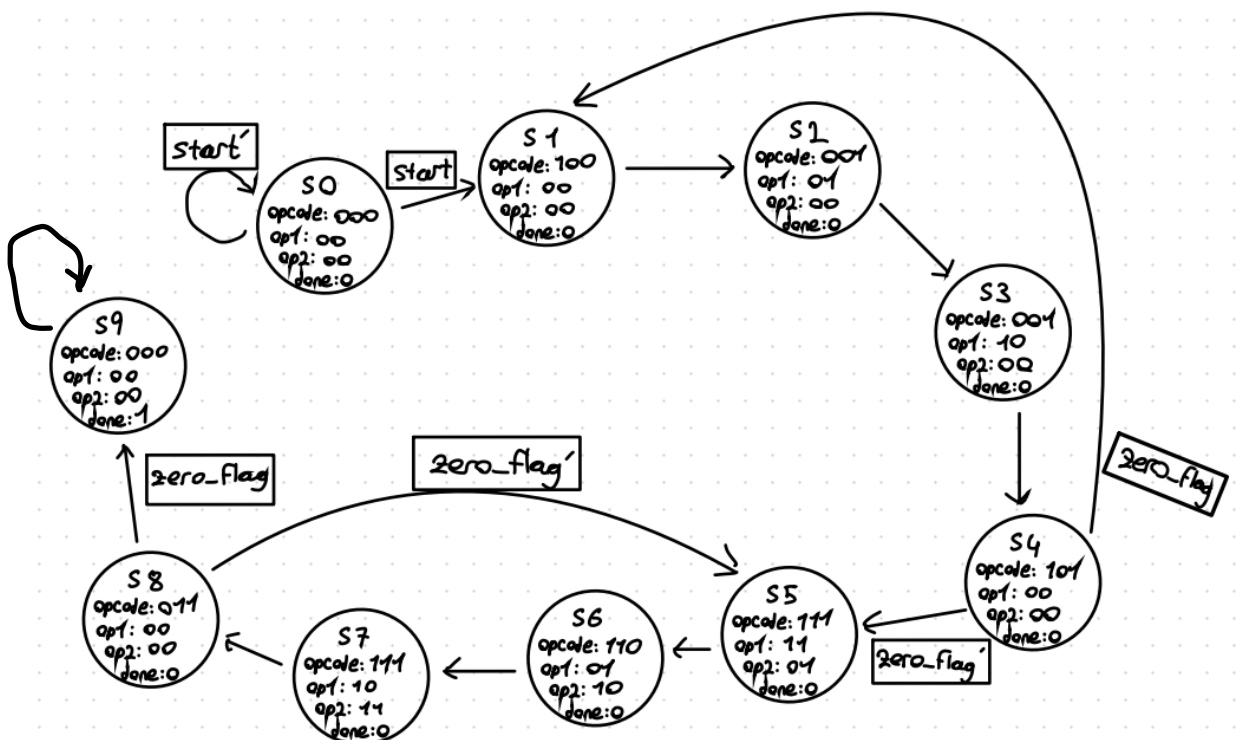

The algorithm of the FSM:

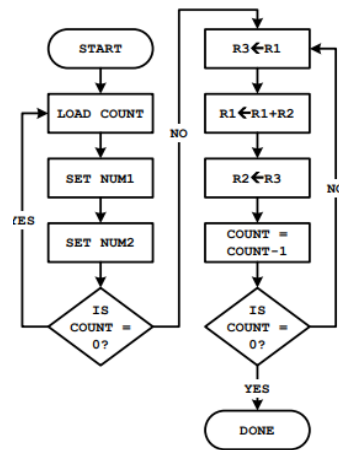

Following this algorithm, the operations in the FSM and the state table is as follows,

START	ZERO_FLAG	Present State	Next State	Opcode	rd_addr1	rd_addr2	Done	Operation	
X	X	X	0000	000	00	00	0	Noop	✓
0	X	0000	0000	000	00	00	0	Noop	✓
1	X	0000	0001	000	00	00	0	Noop	✓
X	X	0001	0010	100	00	00	0	Load Count	✓
X	X	0010	0011	001	01	00	0	Set Num1	✓
X	X	0011	0100	001	10	00	0	Set Num2	✓
X	0	0100	0101	101	00	00	0	R0 ← Count	✓
X	1	0100	0001	101	00	00	0	Check Count	✓
X	X	0101	0110	111	11	01	0	R3 ← R1	✓
X	X	0110	0111	110	01	10	0	R1 ← R1 + R2	✓
X	X	0111	1000	111	10	11	0	R2 ← R3	✓
X	0	1000	0101	011	00	00	0	R0 ← R0 - 1	→ Cont. Calculation
X	1	1000	1001	000	00	00	0	Check Count	
X	X	1001	1001	000	00	00	1	Noop	

## Verilog Codes and Explanations

Datapath Codes:

2-to-4 Line Decoder:

```
1  module decoder_2to4(A,out);
2      input [1:0]A;
3      output reg[3:0]out;
4
5      always @(A)
6      case(A)
7          2'b00: out = 4'b0001;
8          2'b01: out = 4'b0010;
9          2'b10: out = 4'b0100;
10         2'b11: out = 4'b1000;
11
12     endcase
13 endmodule
```

The 2-to-4 Line Decoder takes a 2-bit input which is the wrt\_adder given in the lab manual schematic. After the decoder gets the input, it will activate one of its outputs at a time depending on the input. Each output of the decoder will then go through an AND gate and if the wrt\_en input of the circuit is 1, a register will get the value from the output of a 2-to-1 mux which will be either the previous value of the ALU output or the count value. If the wrt\_en is 0, the register will then hold its previous value.

4-bit register:

```
1  module Register(D,clk,Q);
2      parameter size = 4;
3      input [size-1:0] D;
4      input clk;
5      output reg[size-1:0] Q;
6      initial begin
7          Q=0;
8      end
9      always @(posedge clk)
10     begin
11         Q <= D; //load data
12     end
13 endmodule
..
```

The 4-bit register's aim is to store the values of the algorithm in order to implement it. R0(00) holds the 'count' value, R1(01) stores the Fibonacci number. R2(10) is used to add numbers to R1 and R3(11) is used to copy the numbers of R2 and R1 to implement the algorithm.

4-bit 2-to-1 MUX:

```
module mux2to1(in1,in2,S,mux_out);

    parameter size =4;
    input [size-1:0]in1,in2;
    input S;
    output [size-1:0]mux_out;
    reg [size-1:0]mux_out;

    always@(S,in1,in2)
    if(S == 0)
        begin
            mux_out=in1;
        end
    else
        begin
            mux_out=in2;
        end
    end

endmodule
```

There are four 4-bit 2-to-1 MUXes in the circuit which chooses between loading from the memory state to the registers or holding the previous value in the registers. There is an another MUX which controls the memory state which chooses either the value of 'count' or the ALU output and sends the output to the other MUXes.

4-bit 4-to-1 MUX:

```
module mux4to1(in1,in2,in3,in4,S,mux_out);

    parameter size =4;
    input [size-1:0] in1,in2,in3,in4;
    input [1:0] S;
    output [size-1:0]mux_out;
    reg [size-1:0] mux_out;

    always@(in1,in2,in3,in4,S)
    begin
        if(S[0]==0 && S[1]==0)
            begin
                mux_out=in1;
            end
        else if(S[0]==0 && S[1]==1)
            begin
                mux_out=in3;
            end
        else if(S[0]==1 && S[1]==0)
            begin
                mux_out=in2;
            end
        else
            begin
                mux_out=in4;
            end
        end
    end
endmodule
```

There are two 4-to-1 MUXes in the circuit which both has the same inputs. These MUXes will get their inputs from the registers and choose the value according to the rd\_addr1 and rd\_addr2 inputs which are the select inputs. Then after the registers are chosen, the two outputs will be sent to the ALU as inputs in order to implement the operations.

ALU:

```
module ALU(reg1,reg2,alu_opcode,ALU_out,zero_flag);
parameter size = 4;
input [size-1:0] reg1,reg2;
input [2:0] alu_opcode;
output [size-1:0] ALU_out;
reg [size-1:0] ALU_out;
output zero_flag;
reg zero_flag;
reg [size-1:0] temp;
always @(*)
begin
if (alu_opcode==3'b001)
temp=4'b0001;//set
else if (alu_opcode==3'b010)
temp=reg1+1;//increment
else if (alu_opcode==3'b011)
temp=reg1-1;//decrement
else if (alu_opcode==3'b100)
temp=temp;//load
else if (alu_opcode==3'b101)
temp=reg1;//store
else if (alu_opcode==3'b110)
temp=reg1+reg2;//add
else if (alu_opcode==3'b111)
temp=reg1;//copy
else
temp=temp;//noop
end
always @(*)
begin
ALU_out=temp;
zero_flag = ~(temp);//check result is 0 or not
end
endmodule
```

ALU is the brain and the essential part of the circuit, does all the computations based on an operation code sent to it and then produces the wanted output.

Datapath:

```
module datapath(wrt_addr,rd_addr1,rd_addr2,wrt_en,clk,load_data,alu_opcode,zero_flag,data,count);
parameter size=4;
input [2:0]alu_opcode;
input [1:0]wrt_addr,rd_addr1,rd_addr2;
input [size-1:0]count;
input wrt_en,clk,load_data;
output [size-1:0]data;
output zero_flag;
wire [3:0]out;
wire W0,W1,W2,W3,S0,S1,S2,S3;
wire [size-1:0]Q0,Q1,Q2,Q3,Q4,D0,D1,D2,D3,D4,reg1,reg2;
decoder_2to4 decoder(wrt_addr,out); //decoder
assign W0 = out[0];
assign W1 = out[1];
assign W2 = out[2];
assign W3 = out[3];
//and gates
assign S0=W0&wrt_en;
assign S1=W1&wrt_en;
assign S2=W2&wrt_en;
assign S3=W3&wrt_en;
//2to1 muxes
mux2to1 Mux2to1_0(Q0,D4,S0,D0);
mux2to1 Mux2to1_1(Q1,D4,S1,D1);
mux2to1 Mux2to1_2(Q2,D4,S2,D2);
mux2to1 Mux2to1_3(Q3,D4,S3,D3);
mux2to1 Mux2to1_4(Q4,count,load_data,D4);
//registers
Register R0(D0,clk,Q0);
Register R1(D1,clk,Q1);
Register R2(D2,clk,Q2);
Register R3(D3,clk,Q3);
//4to1 muxes
mux4to1 Mux4to1_1(Q0,Q1,Q2,Q3,rd_addr1,reg1);
mux4to1 Mux4to1_2(Q0,Q1,Q2,Q3,rd_addr2,reg2);
//alu
ALU alu(reg1,reg2,alu_opcode,Q4,zero_flag);
assign data=Q1;
endmodule
```

All the other components of the circuit are gathered together in the datapath to get a reasonable output. The datapath receives signals from the FSM to do the operations. And it sends signals to the FSM in order to get a signal to continue computing or to stop.

## FSM Codes:

### FSM:

```
1  module FSM(start,zero_flag,clk,done,opcode,op1,op2);
2      input zero_flag;
3      input clk,start;
4      reg [3:0]state,nextstate;
5      output reg [2:0]opcode;
6      output reg [1:0]op1,op2;
7      output reg done;
8      parameter S0=4'b0000,S1=4'b0001,S2=4'b0010,S3=4'b0011,S4=4'b0100,S5=4'b0101,S6=4'b0110,S7=4'b0111,S8=4'b1000,S9=4'b1001;
9      always @(posedge clk or posedge start)
10         if(start)
11             state<=nextstate; //fsm will keep continuing as long as start is 1
12         else
13             state<=S0; //if start input is 0, the fsm will begin from state 0
14
15         always @(state or zero_flag or start)
16             begin
17                 op1=2'b00;op2=2'b00;opcode=3'b000;done=0;nextstate=S0;//initil state
18                 case(state)
19                     S0: //reset state
20                         if(start)
21                             begin
22                                 opcode=3'b000;
23                                 op1=2'b00;
24                                 op2=2'b00;
25                                 done=0;
26                                 nextstate=S1;
27                             end
28                         else
29                             nextstate=S0;
30
31                     S1: //load count value
32                         begin
33                             opcode=3'b100;
34                             op1=2'b00;
35                             op2=2'b00;
36                             done=0;
37                             nextstate=S2;
38                         end
39                     S2: //set num1
40                         begin
41                             opcode=3'b001;
42                             op1=2'b01;
43                             op2=2'b00;
44                             done=0;
45                             nextstate=S3;
46                         end
47                     S3: //set num2
48                         begin
49                             opcode=3'b001;
50                             op1=2'b10;
51                             op2=2'b00;
52                             done=0;
53                             nextstate=S4;
54                         end
55                     S4: //check count
56                         begin
57                             opcode=3'b101;
58                             op1=2'b00;
59                             op2=2'b00;
60                             done=1'b0;
61                             if(zero_flag)
62                                 nextstate=S1; //if count is 0 load new count
63                             else
64                                 nextstate=S5; //if count is not 0, continue calculating
65                         end
66                     S5: // R3<-R1
67                         begin
68                             opcode=3'b111; //copy
69                             op1=2'b11; //R3
70                             op2=2'b01; //R1
71                             done=0;
72                             nextstate=S6;
73                         end
74                     S6: //R1<-R1+R2
75                         begin
76                             opcode=3'b110; //add
77                             op1=2'b01;
78                             op2=2'b10;
79                             done=1'b0;
80                             nextstate=S7;
81                         end
82                     S7: //R2<-R3
83                         begin
84                             opcode=3'b111;
85                             op1=2'b10;
86                             op2=2'b11;
87                             done=1'b0;
88                             nextstate=S8;
89                         end
90                     end
91                 end
92             end
93         end
```

```

90         S8: //count<-count-1
91         begin
92             opcode=3'b011;
93             op1=2'b00;
94             op2=2'b00;
95             done=1'b0;
96             if(zero_flag)
97                 nextstate=4'b1001;
98             else
99                 nextstate=4'b0101;
100            end
101        S9: //last state, does no operation, sets done=1
102        begin
103            opcode=3'b000;
104            op1=2'b00;
105            op2=2'b00;
106            done=1'b1;
107            nextstate=4'b1001;
108        end
109    endcase
110 end
111 endmodule

```

The FSM is actually an abstract machine which is responsible of deciding on operations, starting and stopping the calculations in the circuit. Each state in the FSM is actually a step in the algorithm. By starting this algorithm, we get the desired result.

#### FSM\_DECO:

---

```

module FSM_DECO(opcode,op1,op2,alu_opcode,rd_addr1,rd_addr2,wrt_addr,wrt_en,load_data);
    input[2:0]opcode;
    input[1:0]op1,op2;
    output reg [1:0]wrt_addr,rd_addr1,rd_addr2;
    output reg load_data,wrt_en;
    output reg[2:0]alu_opcode;
    always @(opcode,op1,op2)
    begin
        if(opcode==3'b000)//no operation
        begin
            alu_opcode=3'b000;
            rd_addr1=2'b00;
            rd_addr2=2'b00;
            wrt_addr=2'b00;
            wrt_en=1'b0;
            load_data=1'b0;
        end
        else if(opcode==3'b001)//set
        begin
            alu_opcode=3'b001;
            rd_addr1=2'b00;
            rd_addr2=2'b00;
            wrt_addr=op1;
            wrt_en=1'b1;
            load_data=1'b0;
        end
        else if(opcode==3'b010)//increment
        begin
            alu_opcode=3'b010;
            rd_addr1=op1;
            rd_addr2=2'b00;
            wrt_addr=op1;
            wrt_en=1'b1;
            load_data=1'b0;
        end
        else if(opcode==3'b011) //decrement
        begin
            alu_opcode=3'b011;
            rd_addr1=op1;
            rd_addr2=2'b00;
            wrt_addr=op1;
            wrt_en=1'b1;
            load_data=1'b0;
        end
    end
end

```



```

else if(opcode==3'b100) //load
begin
    alu_opcode=3'b100;
    rd_addr1=2'b00;
    rd_addr2=2'b00;
    wrt_addr=op1;
    wrt_en=1'b1;
    load_data=1'b1;
end
else if(opcode==3'b101) //store
begin
    alu_opcode=3'b101;
    rd_addr1=op1;
    rd_addr2=2'b00;
    wrt_addr=2'b00;
    wrt_en=1'b0;
    load_data=1'b0;
end
else if(opcode==3'b110) //add
begin
    alu_opcode=3'b110;
    rd_addr1=op1;
    rd_addr2=op2;
    wrt_addr=op1;
    wrt_en=1'b1;
    load_data=1'b0;
end
else //copy
begin
    alu_opcode=3'b111;
    rd_addr1=op2;
    rd_addr2=2'b00;
    wrt_addr=op1;
    wrt_en=1'b1;
    load_data=1'b0;
end
end
endmodule

```

FSM\_DECO is like the translator of the circuit. It decodes the signals received from the FSM and sends the appropriate signals to the datapath to do the desired operations.

FIBO\_FSM:

```

module FIBO_FSM(start,zero_flag,clk,alu_opcode,rd_addr1,rd_addr2,wrt_addr,wrt_en,load_data,done);
    input clk,start,zero_flag;
    output wrt_en,done,load_data;
    output[1:0]wrt_addr,rd_addr1,rd_addr2;
    output[2:0]alu_opcode;
    wire [2:0]opcode;
    wire [1:0]op1,op2;
    FSM fsm(start,zero_flag,clk,done,opcode,op1,op2);
    FSM_DECO deco(opcode,op1,op2,alu_opcode,rd_addr1,rd_addr2,wrt_addr,wrt_en,load_data);
endmodule

```

FIBO\_FSM connects the FSM to FSM\_DECO in order to send signals to the datapath.

## Top\_level:

```
module top_level(start,clk,done,count,data);
    input start,clk;
    input [3:0]count;
    output done;
    output [3:0]data;
    wire zero_flag;
    wire [2:0]alu_opcode;
    wire [1:0]rd_addr1,rd_addr2,wrt_addr;
    wire wrt_en,load_data;
    wire [3:0]temp;
    assign temp=count-2;
    FIBO_FSM FSM(start,zero_flag,clk,alu_opcode,rd_addr1,rd_addr2,wrt_addr,wrt_en,load_data,done);
    datapath DATAPATH(wrt_addr,rd_addr1,rd_addr2,wrt_en,clk,load_data,alu_opcode,zero_flag,data,temp);
endmodule
```


The last step in the hierarchical design process. Connects the FSM to the Datapath to calculate the Fibonacci sequence.

## Testbench

```
module top_level_tb;
    reg start,clk;
    reg [3:0]count;
    wire done;
    wire [3:0]data;
    top_level fibo(start,clk,done,count,data);
    always
    #10 clk=~clk;
    initial
    begin
        clk=0;start=1;count=4'b0110;

    end
endmodule
```

## Simulation

 

## Conclusion:

After implementing all the components together in the top level design, we can observe that the output of the simulation is correct. The count value is 6 and the output is supposed to be the 6<sup>th</sup> Fibonacci number in the sequence which is 8. We can observe that the output is indeed 8 and the 'done' output is 1 after the operation is done. By finishing this experiment I can say that I am confident with my set of skills in combinational and sequential logic circuit designing concepts.